



DEPARTMENT OF ELECTRICAL ENGINEERING, IIT BOMBAY

EE 344: Electronic Design Lab

Final Project Report

Digital Equalizer

Group Number: BT11

CHANDAN KUMAR(16D070061)

SAARTHAK KAPSE(16D070041)

By prof Siddharth Tallur

05.05.2019(Sunday)

Contents

1 Abstract 2

2 Introduction 2

| | |
|-------------------------------------|---|
| 2.1 Background and Motivation | 2 |
| 2.2 Project Goals | 2 |
| 2.3 Design : Overview | 2 |

3. Concept 3

| | |
|-------------------------------------|---|
| 3.1 basics | 3 |
| 3.2 Theory..... | 3 |
| 3.3 Table for frequency ranges..... | 5 |
| 3.3 Circuit | 5 |
| 3.4 Code | 8 |

4. Conclusion 11

| | |
|---------------------------------------|----|
| 4.1 Results | 11 |
| 4.2 Problem we faced | 11 |
| 4.3 Suggestions for Future work | 11 |

5. Appendix 12

1 Abstract

Recent history has seen significant trend towards digitalization. It has become necessary for engineers accustomed to perform the digital tasks that have traditionally been accomplished in analog. Digital control audio equalizer has been one of the tasks. Our project begins by discussing the needs for equalization and sound quality advantages offers for multi-media systems. Digital equalizer can be designed, tested and modified. The report is to show the advantage of digital equalization over analog like easy verification, it's flexibility, it's reliability and superior sound quality.

2 Introduction

2.1 Background and Motivation:

1. To change the sound profiling and genre of music in favor of listener taste.
2. It is practically useful to adjust the sound of speaker(person).
3. Differentiate between female and male voice: The speech of adult male will have a fundamental frequency from 85 to 180 Hz, and that of a adult female from 165 to 255 Hz

2.2 Project Goals:

Goal of our project is to make digital equalizer using analog filters and digital potentiometer with frequency range from 0 Hz to 20,000 Hz.

2.3 Design : Overview:

For Designing digital equalizer we proceed by making 6 band audio equalizer (ie, filters) having 1 low pass filter, 4 band pass filter of their respective frequencies range and 1 high pass filter to filter out our required sound. Used inverting amplifier to control the gain of each components(frequency bands). Feedback of this inverting amplifier being the digital potentiometer. Basically, Digital potentiometer was used to control the gain of each filter separately from 0 to 10 (the range of the gain). Digital pot will be controlled by Tiva-c launchpad (from texas instrument) and this will be connected to Pc/Laptop via usb. We have chosen band of six filters to be approximately equidistant on the logarithmic scale of frequencies from 20Hz to 20 KHz.

3. Concept

3.1 basics:

In low frequency applications (frequency up to 50-kHz), filters are generally constructed using simple Resistor-Capacitor networks, These filters are function of frequency.

A Low Pass Filter is a circuit that reject all unwanted high frequencies of an electrical signal and pass only those signals wanted by the circuits designer. It only allows low frequency signals from 0Hz to its cut-off frequency f_c to pass while blocking any higher frequency. Cut off frequency in our case is 50Hz.

High Pass Filter – The high pass filter only allows high frequency signals from its cut-off frequency(f_c) and higher to infinity to pass through while blocking any lower frequency.

Band Pass Filter – The band pass filter allows signals within a certain frequency band to pass through while blocking both the lower and higher frequencies on either side of this frequency band.

3.2 Theory;

Equation for low pass filter circuit transfer function is $\frac{1}{1+j\omega RC}$

Cut off frequency(f_c) can and it's phase shift(Φ) is given as

$$*f_c = \frac{1}{2\pi RC} \quad \Phi = -\arctan(2\pi f RC)$$

Equation for high pass filter circuit transfer function is $\frac{R}{R+j\omega C}$

Cut off frequency(f_c) can and it's phase shift(Φ) is given as


$$*f_c = \frac{1}{2\pi RC} \quad \Phi = \arctan(\frac{1}{2\pi f RC})$$

Equation for band pass filter circuit transfer function is

$$f_{cl} = \frac{1}{2\pi R_1 C_1} \quad f_{ch} = \frac{1}{2\pi R_2 C_2}$$


Center frequency can be calculated as $f_0 = \sqrt{f_{cl} * f_{ch}}$

 Bandwidth of any band pass filter can be calculated as $BW = (f_{ch} - f_{cl})$




low pass filter

Low pass filter gain vs frequency plot

 

Band pass filter gain vs frequency plot

 

high-pass filter

High pass filter gain vs frequency plot

* Note-- RC values can be calculated from fc equation.
EE 344 : EDL Final Report


3.3 Table for frequency ranges:

| Filters | 3db Frequency (HZ) | Center frequency (Hz) | Bandwidth (Hz) |
|---------|--------------------------|--------------------------|-------------------|
| HPF | 10400 | -- | - |
| BPF4 | 1500-10400 | 3950 | 8900 |
| BPF3 | 385-2600 | 1000 | 2215 |
| BPF2 | 120-800 | 310 | 680 |
| BPF1 | 50-320 | 126.5 | 270 |
| LPF | 50 | -- | 50 |

3.4 Circuit:


Block Diagram of circuit:-

Here R=10k

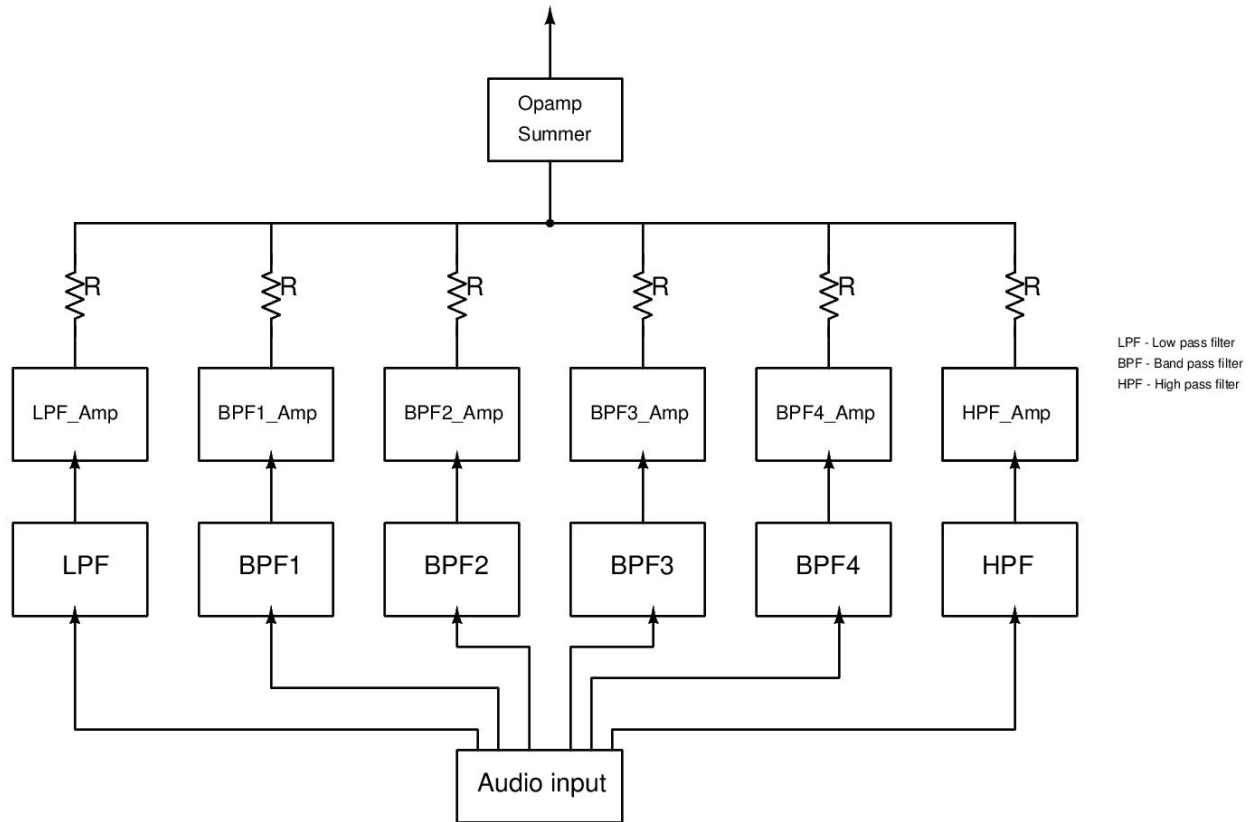


EE 344 : EDL Final Report


LPF:-

 

HPF:-

 


BPF:-

 


EE 344 : EDL Final Report

Amplifier:-

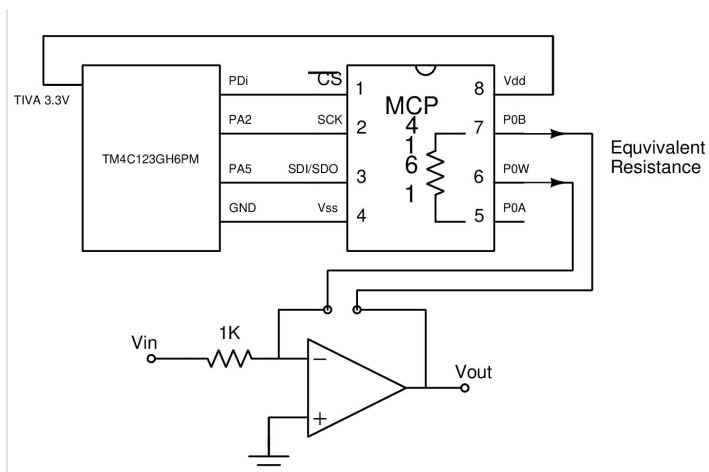

Opamp Summer:-

 

| Filter | R1 | C1 | R2 | C2 |
|--------|------|----------|------|-------|
| BPF1 | 678k | 0.0047uF | 821k | 560pF |
| BPF2 | 594k | 0.0022uF | 713k | 270pF |
| BPF3 | 185k | 0.0022uF | 213k | 270pF |
| BPF4 | 48k | 0.0022uF | 57k | 270pF |

EE 344 : EDL Final Report

| Filter | R1 | C1 | R_1 | R_2 |
|--------|-------|--------|------|------|
| LPF | 33k | 0.01uF | 1.2 | 8.2 |
| HPF | 15.9k | 0.001u | 5.6k | 1.2k |

3.5 Code:

Code for digital potentiometer control is

Acknowledgment-Shashank

```
#include <stdint.h>
#include <stdlib.h>
#include "TM4C123GH6PM.h"
#define SSI0_SR_R      (*((volatile unsigned long *)0x4000800C))
```

```

#define SSI0_CPSR_R      (*((volatile unsigned long *)0x40008010))
#define SSI0_CC_R        (*((volatile unsigned long *)0x40008FC8))
#define SSI_CR0_SCR_M    0x0000FF00 // SSI Serial Clock Rate
#define SSI_CR0_SPH      0x00000080 // SSI Serial Clock Phase
#define SSI_CR0_SPO      0x00000040 // SSI Serial Clock Polarity
#define SSI_CR0_FRF_M    0x00000030 // SSI Frame Format Select
#define SSI_CR0_FRF_MOTO 0x00000000 // Freescale SPI Frame Format
#define SSI_CR0_DSS_M    0x0000000F // SSI Data Size Select
#define SSI_CR0_DSS_8    0x00000007 // 8-bit data
#define SSI_CR1_MS       0x00000004 // SSI Master/Slave Select
#define SSI_CR1_SSE      0x00000002 // SSI Synchronous Serial Port Enable
#define SSI_SR_RNE       0x00000004 // SSI Receive FIFO Not Empty
#define SSI_SR_TNF       0x00000002 // SSI Transmit FIFO Not Full
#define SSI_SR_TFE       0x00000001 // SSI Transmit FIFO Empty
#define SSI_CPSR_CPSDVSR_M 0x000000FF // SSI Clock Prescale Divisor
#define SSI_CC_CS_M      0x0000000F // SSI Baud Clock Source
#define SSI_CC_CS_SYSPLL 0x00000000 // Either the system clock (if the
// PLL bypass is in effect) or the
// PLL output (default)
#define SYSCTL_RCGC1_R    (*((volatile unsigned long *)0x400FE104))
#define SYSCTL_RCGC2_R    (*((volatile unsigned long *)0x400FE108))
#define SYSCTL_RCGC1_SSI0 0x00000010 // SSI0 Clock Gating Control
#define SYSCTL_RCGC2_GPIOA 0x00000001 // port A Clock Gating Control
#define APINT_R           (*((volatile unsigned long *)0xE000ED0C))

```

```

void ssi_Init(void);
void timer0A_delayMs(int ttime);
void ss_pd0(int c0);
void ss_pd1(int c1);
void ss_pd2(int c2);
void ss_pd3(int c3);
void ss_pd6(int c6);
void ss_pd7(int c7);

```

```
int i=0,r0_pd0,r1_pd1,r2_pd2,r3_pd3,r6_pd6,r7_pd7;
```

```

int main(void){
    ssi_Init();
    volatile unsigned long delay;
    /***** PD 0, 1, 2, 3, 6, 7*****/
    SYSCTL_RCGC2_R |= 0x00000008; //enable clock
    delay = SYSCTL_RCGC2_R; //delay needed for above to finish
    GPIO_PORTD_CR_R = 0xCF; //enable writing in it
    GPIO_PORTD_AMSEL_R &= 0x30; //disable analog
    GPIO_PORTD_PCTL_R = 0x00; //regular digital

```

```

GPIO_PORTD_DIR_R = 0xCF;      // output
GPIO_PORTD_AFSEL_R &= 0x30;   //disable alt function
GPIO_PORTD_DEN_R = 0xCF;     //enable digital function
GPIO_PORTD_DATA_R = 0xCF;

while(1)
{
    ss_pd0(1); //HPF
    ss_pd1(1); //BPF4
    ss_pd2(1); //BPF3
    ss_pd3(255); //BPF2
    ss_pd6(255); //BPF1
    ss_pd7(1); //LPF
}
}
////////////////////////////////////
void ssi_Init(void){
    volatile unsigned long delay2;
    SYSCTL_RCGC1_R |= SYSCTL_RCGC1_SSI0; // activate SSI0
    SYSCTL_RCGC2_R |= SYSCTL_RCGC2_GPIOA; // activate port A
    GPIO_PORTA_AFSEL_R |= 0x3C;          // enable alt funct on PA2,3,5
        // configure PA2,3,5 as SSI
    GPIO_PORTA_PCTL_R = (GPIO_PORTA_PCTL_R & 0xFF0000FF)+0x00222200;
    GPIO_PORTA_DEN_R |= 0x3C;           // enable digital I/O on PA2,3,4,5
    GPIO_PORTA_AMSEL_R &= ~0x3C;       // disable analog functionality on
PA2,3,5,6,7
    SSI0_CR1_R &= ~SSI_CR1_SSE;        // disable SSI
    SSI0_CR1_R &= ~SSI_CR1_MS;         // master mode
        // configure for system clock/PLL baud clock source
    SSI0_CC_R = (SSI0_CC_R&~SSI_CC_CS_M)+SSI_CC_CS_SYSPLL;
        // clock divider for 2 MHz SSIClk (16 MHz PIOSC/2)
    SSI0_CPSR_R = (SSI0_CPSR_R&~SSI_CPSR_CPSDVSR_M)+2;
    SSI0_CR0_R &= ~(SSI_CR0_SCR_M |    // SCR = 0 (2 Mbps data rate)
        SSI_CR0_SPH |                // SPH = 0
        SSI_CR0_SPO);                // SPO = 0
        // FRF = Freescale format
    SSI0_CR0_R = (SSI0_CR0_R&~SSI_CR0_FRF_M)+SSI_CR0_FRF_MOTO;
        // DSS = 16-bit data
    SSI0_CR0_R = (SSI0_CR0_R&~SSI_CR0_DSS_M)+SSI_CR0_DSS_16;
    SSI0_CR1_R |= SSI_CR1_SSE;         // enable SSI
}

void ss_pd0(int c0)
{

```

```

    GPIO_PORTD_DATA_R &= ~(0x01);
    SSI0_DR_R = c0;
    while((SSI0_SR_R & 0x01)==0x00){}; // wait until data has finished
transmitting
    timer0A_delayMs(10);
    GPIO_PORTD_DATA_R |= 0x01;
}

```

```

void ss_pd1(int c1)
{
    GPIO_PORTD_DATA_R &= ~(0x02);
    SSI0_DR_R = c1;
    while((SSI0_SR_R & 0x01)==0x00){}; // wait until data has finished
transmitting
    timer0A_delayMs(10);
    GPIO_PORTD_DATA_R |= 0x02;
}

```

```

void ss_pd2(int c2)
{
    GPIO_PORTD_DATA_R &= ~(0x04);
    SSI0_DR_R = c2;
    while((SSI0_SR_R & 0x01)==0x00){}; // wait until data has finished
transmitting
    timer0A_delayMs(10);
    GPIO_PORTD_DATA_R |= 0x04;
}

```

```

void ss_pd3(int c3)
{
    GPIO_PORTD_DATA_R &= ~(0x08);
    SSI0_DR_R = c3;
    while((SSI0_SR_R & 0x01)==0x00){}; // wait until data has finished
transmitting
    timer0A_delayMs(10);
    GPIO_PORTD_DATA_R |= 0x08;
}

```

```

void ss_pd6(int c6)
{
    GPIO_PORTD_DATA_R &= ~(0x40);
    SSI0_DR_R = c6;
    while((SSI0_SR_R & 0x01)==0x00){}; // wait until data has finished
transmitting
    timer0A_delayMs(10);
    GPIO_PORTD_DATA_R |= 0x40;
}

```

```

}
void ss_pd7(int c7)
{
    GPIO_PORTD_DATA_R &= ~(0x80);
    SSI0_DR_R = c7;
    while((SSI0_SR_R & 0x01) == 0x00){}; // wait until data has finished
transmitting
    timer0A_delayMs(10);
    GPIO_PORTD_DATA_R |= 0x80;
}

void timer0A_delayMs(int ttime)
{
    int i;
    SYSCTL_RCGCTIMER_R |= 1; /* enable clock to Timer Block 0 */

    TIMER0_CTL_R = 0; /* disable Timer before initialization */
    TIMER0_CFG_R = 0x04; /* 16-bit option */
    TIMER0_TAMR_R = 0x02; /* periodic mode and down-counter */
    TIMER0_TAILR_R = 16000 - 1; /* Timer A interval load value register */
    TIMER0_ICR_R = 0x1; /* clear the TimerA timeout flag */
    TIMER0_CTL_R |= 0x01; /* enable Timer A after initialization */

    for(i = 0; i < ttime; i++) { while ((TIMER0_RIS_R & 0x1) == 0); /* wait for
TimerA timeout flag */
        TIMER0_ICR_R = 0x1; /* clear the TimerA timeout flag */    }    }

```

EE 344 : EDL Final Report

4 Conclusion:

4.1 Results :

1. Bass: We got bass at our output (Speaker/earphone) When we amplified the 1st and 2nd band pass filter of frequencies ranges 50 Hz - 120Hz and 12 Hz-385 Hz respectively only.
2. Only instrumental sound: Since, Fundamental frequency of most of the instruments lies between 400 Hz to 4 KHz. We did hear the sound of instruments when 3rd and 4th band pass filter were amplified only.
For more detail:

https://docs.google.com/spreadsheets/d/1JDkWlz62iOTgQhlCyl07U2Bhliu1yrkgU3AIqtTI_qI/edit?usp=sharing

3. Only voice sound: ` Normal vocal sound of human are of frequency range 85 Hz to 255 Hz. So, we were able to hear the sound of the person singing.

4.2 Problems faced:

1. During making the inverting amplifier it was somehow showing the offset on Ua741 op-amp. so, we moved to TL071.
2. LPF and HPF gain was not equal to 1. So, we added an extra resistor at feedback.
3. On completion of analog it was giving some noise because of wire looping and stereo input jack.
4. Since, Output of filters was not coming correctly at our initial resistor and capacitor value calculated. We had to adjust accordingly. So, that it can give our desired output value at different frequencies.

4.3 Suggestions for Future work:

1. Gui:

We can implement gui based digital equalizer for easy control of the digital pots instead of changing the value of resistor of digital pots in laptop.


EE 344 : EDL Final Report

2. Higher order filter:

We can implement higher order filters for more feathering of the Sound Like reverse sound, rotating sound, high tone, low tone and 3-D sounds genres.

5 Appendix:

 Our Final circuit on breadboard looked something like this :



End report